

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION SP/2024)

CLASS: B.TECH
BRANCH: CSE/AI ML/ECE/EEE

SEMESTER : II
SESSION : SP/2024

SUBJECT: EE101 BASIC OF ELECTRICAL ENGINEERING


TIME: 02 Hours

FULL MARKS: 25


INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

- | | | CO | BL |
|--|-----|----|----|
| Q.1(a) Define the terms: (i) Independent Source (ii) Dependent Source | [2] | 1 | 1 |
| Q.1(b) Determine the loop currents I_1, I_2, I_3, I_4 for the network shown in the figure below: | [3] | 1 | 3 |

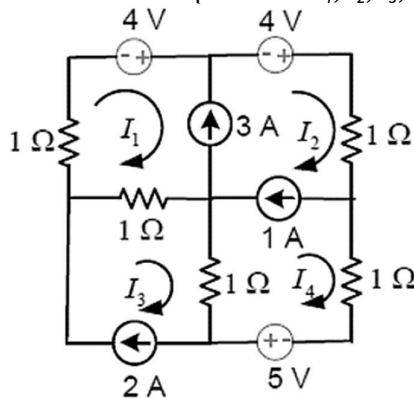

- | | | | |
|--|-----|---|---|
| Q.2(a) Explain the concept of a Super node and state the limitations associated in this analysis? | [2] | 1 | 2 |
| Q.2(b) Using the Star/Delta conversion technique, determine the current flowing between the terminals A and B when a 5V dc source is connected between them? | [3] | 1 | 3 |

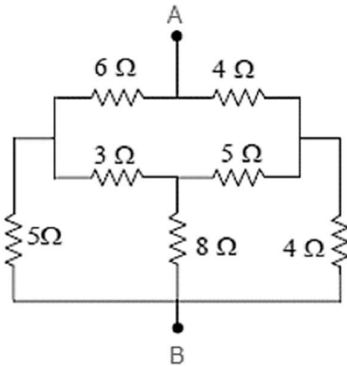

- | | | | |
|--|-----|---|---|
| Q.3(a) Define the concept of a power triangle with a neat phasor diagram? | [2] | 2 | 1 |
| Q.3(b) Four emfs, $e_1 = 100\sin(\omega t)$, $e_2 = 80\sin(\omega t - \pi/3)$, $e_3 = 90\sin(\omega t + \pi/4)$ and $e_4 = 120\cos(\omega t)$ are induced in four coils connected in series. Assuming that the current ($i = I\sin(\omega t)$) flowing in the circuit lags e_4 , calculate the resultant emf and its phase difference with e_1 and e_2 . Draw a neat phasor diagram? | [3] | 2 | 3 |
| Q.4(a) Define the terms: (i) Average Value (ii) RMS Value (iii) Form Factor (iv) Phase Difference | [2] | 2 | 1 |
| Q.4(b) In a series RLC circuit, an AC voltage of $120e^{j\omega t}$ V is applied at a frequency of 400 rad/sec. The input current leads the voltage by 63.5 degrees. Calculate the value of 'R' if $L = 0.025\text{H}$ and $C = 50\mu\text{F}$. What are the voltage drops across L and C ? Draw a neat phasor diagram? | [3] | 2 | 3 |

- Q.5(a) Explain the concept of a series resonance through the use of impedance-frequency curve. Plot the Impedance frequency curve also? [2] 2 2
- Q.5(b) A series resonant RLC circuit has a resonant frequency of 80K rad/sec and a quality factor of 8. Calculate the bandwidth, the upper cut-off and lower cut-off frequencies? [3] 2 3

:::::23/02/2024 E:::::